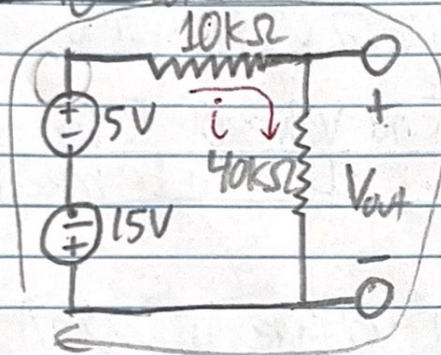


MECHATRONICS HW 1

Nathan
Delos
Santos

① Find: V_{out}



• KVL: $15V - 5V + i(10k\Omega) + i(40k\Omega) = 0$


$10V = -50k\Omega \cdot i$

$i = -0.0002A = -0.2mA$


• Ohm's Law: $V_{out} = V_{40k\Omega} = i \cdot 40k\Omega$

$V_{out} = -8V$

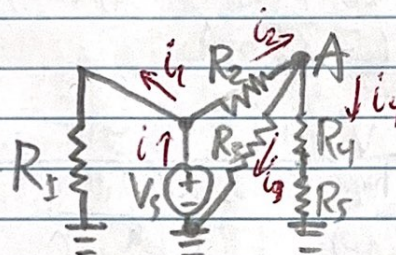② • $R_1 = 1k\Omega$ • $R_2 = 2k\Omega$
• $R_3 = 3k\Omega$ • $R_4 = 4k\Omega$
• $R_5 = 1k\Omega$ • $V_s = 10V$



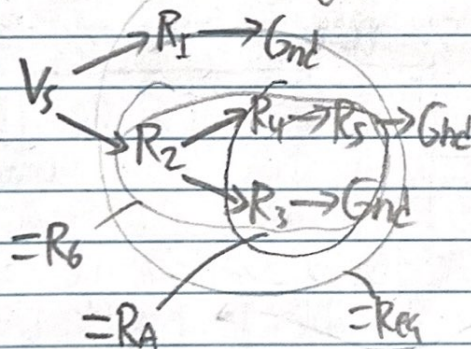Find: total equivalent resistance between V_s & gnd



• $R_{eq} = R_1 \parallel R_5 \parallel (R_2 \parallel (R_3 \parallel (R_4 + R_5)))$

• $R_6 = R_2 + \frac{1}{\frac{1}{R_3} + \frac{1}{(R_4 + R_5)}}$

• $R_{eq} = R_1 \parallel R_6 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_6}} \Rightarrow R_{eq} = \frac{31}{39}k\Omega \approx 0.795k\Omega$

Find: V_A & current thru R_5


• Voltage division between R_2 & $(R_3 \parallel (R_4 + R_5))$

• $V_s = V_{R_2} + V_A \Rightarrow V_s = i_2 R_2 + V_A$
• $V_s = i_2 (R_2 + R_A) \Rightarrow i_2 = \frac{V_s}{R_2 + R_A}$
• Plugging in: $V_s = \frac{V_s}{R_2 + R_A} R_2 + V_A \Rightarrow V_s (1 - \frac{R_2}{R_2 + R_A}) = V_A \Rightarrow V_A = V_s \frac{R_A}{R_2 + R_A} \Rightarrow V_A \approx 4.84V$

• Current thru R_5 is i_4

$V_A = i_4 (R_4 + R_5) \Rightarrow i_4 = \frac{V_A}{R_4 + R_5} \Rightarrow i_4 = 0.4677mA$

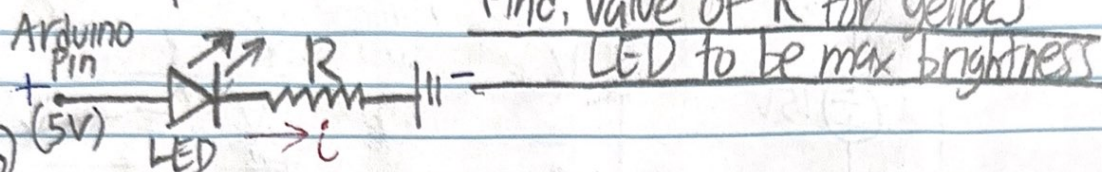- ④ on next pg, forward voltage of red & yellow leds.
 • red: 1.6-2.0V • yellow: 2.1-2.2V, so will use 2.0V
 for the problem, since is yellow




- ⑥ note, current at forward voltage is 20mA
 • so $i = 20\text{mA}$

$$5V = V_{\text{led}} + iR \Rightarrow 5V = 2.0V + 20\text{mA}(R) \Rightarrow R = 150\Omega$$

• If use higher resistor, LED is dimmer. Lower, LED might burn

⑦ Consider 4 LEDs in parallel

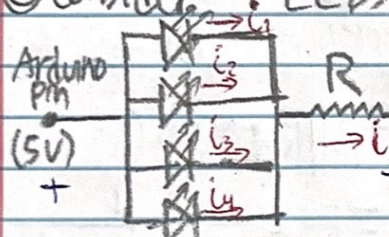

$$i_1 = i_2 = i_3 = i_4 = i_{\text{led}}, \text{ so } i = 4 \cdot i_{\text{led}}$$

$$5V = V_{\text{led}} + iR \Rightarrow 5V = 2.0V + 80\text{mA}(R)$$

$$R = 37.5\Omega \approx 38\Omega$$

While it is best to power LEDs in parallel, connecting their common grounds to one resistor, like above, can be problematic, since the resistor might not be able to handle the current (more accurately, the power) going thru it

- ⑧ It is not advisable to connect 4 yellow leds in series if powered by an arduino pin. The arduino can only provide max 5V, and 4 yellow leds would require 8V drop. The leds wouldn't be fully powered

In addition, it's not good to wire lights in series. If one goes out, all go out, and it becomes hard to tell which one is busted

[1]“The Forward Voltages of Different LEDs | CircuitBread,” *The Forward Voltages of Different LEDs | CircuitBread*. <https://www.circuitbread.com/ee-faq/the-forward-voltages-of-different-leds>

[2]“LED - Basic Yellow 5mm - COM-09594 - SparkFun Electronics,” *www.sparkfun.com*.
<https://www.sparkfun.com/products/9594#:~:text=It%20has%20a%20typical%20forward>

```

clc;
clear;
close all;

digitsDesired = 3; %%enter digits here!
primes = primesUpToDigit(digitsDesired) %%call it here!!!
sprintf("Sum of primes up to %d digits: %d",digitsDesired, sum(primes))

function [primes] = primesUpToDigit(digits)
    maxNum = 10^digits - 1; %for example, if want 3 digits, then get 10^3 -1 =
    1000 -1 = 999, the largest 3 digit numbner
    primes = [2,3]; %will get populated as the loop progresses
    startNumber = primes(end)+1; %will start collecting at the end of the
    primes list + 1, so in this case, at 3+1=4

    for i = startNumber:maxNum
        for ii = 1:length(primes)
            if mod(i,primes(ii)) == 0 %modulo to check for remainders of
dividing i by primes(ii)
                %if remainder is 0, then that number is divisible, so break
                %loop, and skip this number
                break
            end
        end
        %if it reached the end of the list without breaking loop (for ii),
    then
        %that number was not found to be divisible by anything, so its prime
        %this works because you keep adding more and more numbers to the list,
        %so bigger numbers have more factors to check against
        if ii == length(primes)
            primes(end+1) = i;
        end
    end
    primes;
end

```

```
primes =
```

Columns 1 through 13

2	3	5	7	11	13	17	19	23	29	31	37	41
---	---	---	---	----	----	----	----	----	----	----	----	----

Columns 14 through 26

43	47	53	59	61	67	71	73	79	83	89	97	101
----	----	----	----	----	----	----	----	----	----	----	----	-----

Columns 27 through 39

103	107	109	113	127	131	137	139	149	151	157	163	167
-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----

Columns 40 through 52

```

173 179 181 191 193 197 199 211 223 227 229 233 239
Columns 53 through 65

241 251 257 263 269 271 277 281 283 293 307 311 313
Columns 66 through 78

317 331 337 347 349 353 359 367 373 379 383 389 397
Columns 79 through 91

401 409 419 421 431 433 439 443 449 457 461 463 467
Columns 92 through 104

479 487 491 499 503 509 521 523 541 547 557 563 569
Columns 105 through 117

571 577 587 593 599 601 607 613 617 619 631 641 643
Columns 118 through 130

647 653 659 661 673 677 683 691 701 709 719 727 733
Columns 131 through 143

739 743 751 757 761 769 773 787 797 809 811 821 823
Columns 144 through 156

827 829 839 853 857 859 863 877 881 883 887 907 911
Columns 157 through 168

919 929 937 941 947 953 967 971 977 983 991 997

```

`ans =`

```
"Sum of primes up to 3 digits: 76127"
```

Published with MATLAB® R2022b

primeNumbersCollector.cpp

```

1  #include <iostream>
2  #include <vector> //so can add elements to arrays at runtime
3  #include <cmath>
4
5  using namespace std;
6  int desiredDigits = 3;
7
8  vector<int> primeFinder(int digitCount){
9      int maxNum = pow(10,digitCount) - 1;
10     //for example, if want 3 digits, then get 10^3 -1 = 1000 -1 = 999, the largest 3 digit
    numbrer
11     vector<int> primes = {2,3};
12
13     //cout << "maxNum: " << maxNum << " \n";
14     int ii; //need to declare this outside the loop so that stuff outside the loop can access
    it
15
16     //sizeof(primes)/sizeof(primes[0]) is the length of the array, primes with plain c++
    arrays
17     //primes.size() is how it is done with vectors in c++
18     //will start collecting at the end of the primes list + 1, so in this case, at 3+1=4
19     for(int i = primes[primes.size() - 1] +1; i<=maxNum ; i++){
20         //cout << "i = " << i << " \n";
21         for(ii = 0;ii<primes.size();ii++){
22             if(i % primes[ii] == 0){
23                 break;
24                 //modulo to check for remainders of dividing i by primes(ii)
25                 //if remainder is 0, then that number is divisible, so break
26                 //loop, and skip this number
27             }
28         }
29         //cout << "checked, ii = " << ii << " , length of primes: " << primes.size() << " \n";
30         //if it reached the end of the list without breaking loop (for ii), then
31         //that number was not found to be divisible by anything, so its prime
32         //this works because you keep adding more and more numbers to the list,
33         //so bigger numbers have more factors to check against
34         if(ii == primes.size()){
35             primes.push_back(i);
36         }
37     }
38     return primes;
39 }
40
41 int main(){
42     int sumOfPrimes=0;
43     vector<int> foundPrimes = primeFinder(desiredDigits);
44     cout << "Primes Up To " << desiredDigits << " Digits: \n";
45     for (const int &i : foundPrimes) {
46         cout << i << " , ";
47         sumOfPrimes += i;
48     }
49     cout << "\n";
50     cout << "Sum Of Primes Up To " << desiredDigits << " Digits: "<< sumOfPrimes << "\n";

```

```
51 |     return 0;  
52 | }  
53 |  
54 |
```